

## Boolean Algebra

$$x + 0 = x$$

$$x * 0 = 0$$

$$x + 1 = 1$$

$$x * 1 = x$$

$$x + x = x$$

$$x * x = x$$

$$x + x' = 1$$

$$x * x' = 0$$

$$(x')' = x$$

\* Distributivity:

$$(x + y) * (z + w) = xz + xw + yz + yw$$

$$x + yz = (x + y)(x + z)$$

\* DeMorgan's Law:

$$(x + y)' = x' * y'$$

$$(x' * y')' = x + y$$

$$(x' + y)' = x * y'$$

Ex1:

"Common Factor"

①

$$f = x + x \cdot y \quad \leftarrow 2 \text{ logic Gates}$$

$$= x \cdot (1 + y)$$

$$f = x$$

$\leftarrow 0$  logic Gates

Ex2:

"Distributivity"

②

$$\square + \square'$$

$$x + x' y$$

$$y + y' z$$

$$f = x + x' y$$

$$= (x + x') \cdot (x + y)$$

$$f = x + y$$

Ex3:

"Common Factor" + "Distributivity"

③

$$f = (x)y + (x)y'z$$

$$= x(y + y'z)$$

$$= x(y + y')(y + z)$$

$$f = x(y + z)$$

$$F = \underline{A}BC + \underline{A}BC' + A'B$$

$$= AB(C + C') + A'B$$

$$= AB * 1 + A'B$$

$$= \underline{A}B + \underline{A'B}$$

$$= \underline{B}A + \underline{BA'}$$

$$= B(A + A')$$

$$= B * 1$$

$$= B$$

Distributivity note:

$$x + x' = 1$$

$$x * 1 = x$$

Comm

Distributivity

$$x + x' = 1$$

$$x * 1 = x$$

$$F = xy + x'y'$$

$$= x(y + y')$$

$$= x$$

$$F = xy + xz$$

$$= x(y + z)$$

$$P = (A + B)'(A' + B')$$

$$= (A'B') (A' + B')$$

$$= \boxed{A'A'}B' + A'\boxed{B'B'}$$

$$= A'B' + A'B'$$

$$= A'B'(1+1)$$

$$= A'B'$$

DeMorgans' law

Distributivity

$$x \cdot x = x$$

Distr.

$$1+1=1$$

$$F = (A + B' + AB')(AB + A'C + BC)$$

$$= (\underline{A} + \underline{A}B' + B') \cdot (AB + A'C + BC)$$

$$= (A(\cancel{1+B'}) + B') \cdot (AB + A'C + BC)$$

$$= (A * 1 + B') \cdot (AB + A'C + BC)$$

$$= (A + B')(AB + A'C + BC)$$

$$= \boxed{AAB} + \cancel{AA'C} + ABC + \cancel{ABB} + A'B'C + \cancel{BB'C}$$

$$= \boxed{AAB} + ABC + A'B'C$$

$$= \underline{AB} + \underline{ABC} + A'B'C$$

$$= AB(\cancel{1+C}) + A'B'C$$

$$= AB * 1 + A'B'C$$

$$\boxed{F = A.B + A'.B'.C}$$

6 Logic Gates



$$F = P'XY + PX'Y + \underline{PXY'} + \underline{PXY}$$

$$= P'xy + P\bar{x}y + Px(y' + y)$$

$$= P'xy + P\bar{x}y + Px \cdot 1$$

$$= P'xy + \underline{P\bar{x}y} + \underline{Px}$$

$$= P'xy + P(\bar{x}y + x)$$

$$= P'xy + P(\cancel{\bar{x} + x})(y + x)$$

$$= P'xy + P(y + x)$$

$$= P'x\underline{y} + P\underline{y} + Px$$

$$= yP'x + yP + Px$$

$$= y(\cancel{P'x + P}) + Px$$

$$= y(\cancel{P' + P})(x + P) + Px$$

$$F = y \cdot (x + P) + \underline{P} \cdot x$$

$$F = yx + yP + Px$$

4 Logic Gates

5 Logic Gates

# Exercise 11-2

Given the following Boolean expression, simplify it to a minimum number of literals using the Boolean algebra. Please mention the applied rules.


$$((A+B)(B'+C'+D')) + B'C'(A+B'+C) + A'C + D$$

Hint: The circuit of the simplified expression consists of zero gates.

$$\begin{aligned}
 F &= (A+B)(B'+C'+D') + B'C'(A+B'+C) + A'C + D \quad \text{Dist} \\
 &= AB' + AC' + AD' + \cancel{BB'} + BC' + BD' + AB'C' + \cancel{B'B'C'} + \cancel{B'C'C} + A'C + D \\
 &= \underline{AB'} + AC' + AD' + \underline{BC'} + BD' + \underline{AB'C'} + \underline{B'C'} + A'C + D \\
 &= \underline{AB'} + \underline{AB'C'} + \underline{C'B} + \underline{C'B'} + AC' + AD' + BD' + A'C + D \\
 &= \underline{AB'}(1 + \cancel{C}) + \cancel{C}(B + B') + AC' + AD' + BD' + A'C + D \\
 &= \underline{AB'} + \underline{C'} + \underline{AC'} + AD' + BD' + A'C + D \\
 &= \underline{AB'} + C' + C'A + AD' + BD' + A'C + D \\
 &= \underline{AB'} + C'(1 + A) + AD' + BD' + A'C + D \\
 &= \underline{AB'} + \underline{C'} + \underline{AD'} + BD' + \underline{A'C} + \underline{D} \\
 &= \underline{AB'} + BD' + \underline{D} + \underline{DA} + \underline{C'} + \underline{CA} \\
 &= \underline{AB'} + BD' + (\underline{D} + \underline{D})(\underline{D} + \underline{A}) + (\underline{C'} + \underline{C})(\underline{C'} + \underline{A}) \\
 &= \underline{AB'} + BD' + D + \underline{A + A'} + C' = \underline{1}
 \end{aligned}$$

Exercise 11-3

Given the following circuit

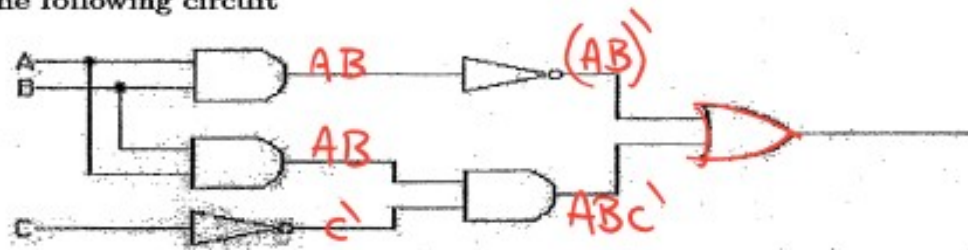

- Determine the boolean expression of the circuit
- Determine the truth table of the circuit.

a)  $F = (AB)' + ABC'$   $= A' + B' + ABC'$

b)

A	B	C	P
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0


$A=0$   
 $B=0$   
 $C=0$   
 $A=0$   
 $B=0$   
 $C=1$

$$F = A' + B' + ABC'$$

$A=1$   
 $B=1$   
 $C=0$

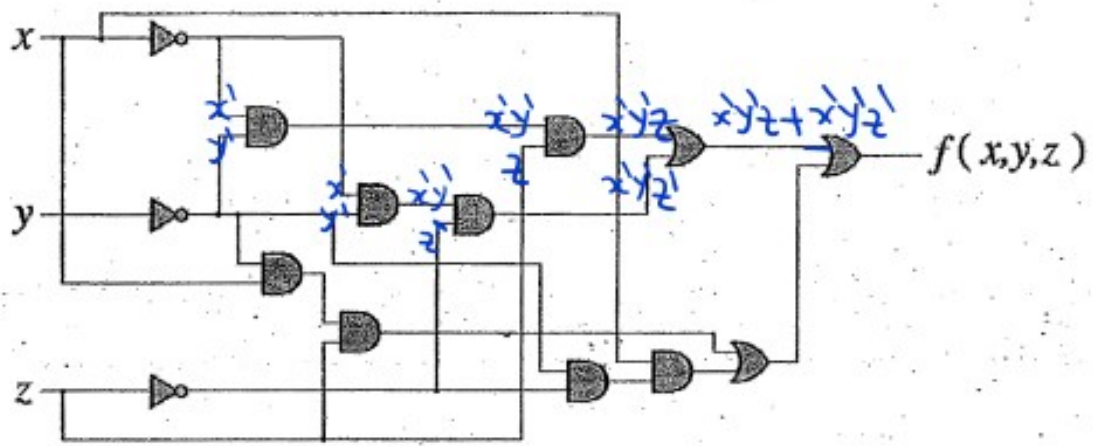$\downarrow$   
 $0 + 0 + (1 \cdot 1 \cdot 1) = 1$





### Exercise 7

(3+3+4+2=12 Marks)

Given the following truth table, where A, B are the input variables and X, Y and Z are the output variables.

N	A	B	X	Y	Z	R
0	0	0	0	1	0	2 3 4 5
1	0	1	0	1	1	
2	1	0	1	0	0	
3	1	1	1	0	1	

$$R = N + 2$$

a) Use the sum-of-products algorithm to find the Boolean expressions that describe the output of the truth table.

b) What is the functionality of the circuit?

### Exercise 7

(5+4+5=14 Marks)

Given the following truth table, where A, B are the input variables and X, Y, and Z are the output variables.

N	A	B	X	Y	Z	R
0	0	0	0	0	0	0 1 2 3
1	0	1	0	0	1	
2	1	0	0	1	1	
3	1	1	1	1	1	

$$R = 2 - 1$$

a) Use the sum-of-products algorithm to find the Boolean expressions that describe the output of the truth table.

b) What is the functionality of the circuit?